

# Quantified Boolean Logic

Extension of propositional logic with **boolean quantifiers**.

We write

$\exists A F$  as an abbreviation of  $F[A/0] \vee F[A/1]$

$\forall A F$  as an abbreviation of  $F[A/0] \wedge F[A/1]$

Abbreviations can be nested, and then they are “unfolded” inside-out:

$\exists A \forall B (A \wedge B)$

abbreviates  $\exists A (A \vee 0) \wedge (A \vee 1)$

which abbreviates  $((0 \vee 0) \wedge (0 \vee 1)) \vee ((1 \vee 0) \wedge (1 \vee 1))$


Intuitively,  $\exists A \forall B (A \wedge B)$  “means”

there exists a truth value for  $A$  such that for every truth value for  $B$  the formula  $(A \wedge B)$  becomes true.
 
# Modelling circuits with QBL

Gates as boolean formulas

Stable states as satisfying truth assignments



**not**(a, b)  $\equiv \neg a \leftrightarrow b$


**and**(a, b, c)  $\equiv (a \wedge b) \leftrightarrow c$

**or**(a, b, c)  $\equiv (a \vee b) \leftrightarrow c$

**xor**(a, b, c)  $\equiv ((\neg a \wedge b) \vee (a \wedge \neg b)) \leftrightarrow c$


 
## Combining gates means combining formulas

Combine gates with  $\wedge, \exists$  (and renaming of atomic formulas)



$$R(x, y, q, r, s) = \exists w R_1(x, y, w, q) \wedge R_2(y, w, r, s)$$

## A full adder

  


**full\_adder**(a, b, s, cin, cout)  $\equiv$

$$\exists w_1 \exists w_2 \exists w_3 \mathbf{xor}(a, b, w_1) \wedge \mathbf{xor}(w_1, \mathbf{cin}, s) \wedge \mathbf{and}(a, b, w_2) \wedge \mathbf{and}(\mathbf{cin}, w_1, w_3) \wedge \mathbf{or}(w_3, w_2, \mathbf{cout})$$
 
## A $n$ -bit ripple-carry adder

$$\begin{array}{r}
 c_2 \quad c_1 \quad cin \quad (= 0) \\
 a_2 \quad a_1 \quad a_0 \\
 + \quad b_2 \quad b_1 \quad b_0 \\
 \hline
 cout \quad s_2 \quad s_1 \quad s_0
 \end{array}$$

Wire together  $n$  1-bit adders where  $i$ -th carry-out is  $i+1$ -st carry-in, first carry is the carry-in and last is the carry-out.



We obtain the formula

$$\begin{aligned}
 \text{adder}_n(a_0, \dots, a_{n-1}, b_0, \dots, b_{n-1}, s_0, \dots, s_{n-1}, cin, cout) \equiv \\
 \exists c_0 \exists c_1 \dots \exists c_n (c_0 \leftrightarrow cin) \wedge (c_n \leftrightarrow cout) \wedge \\
 \bigwedge_{i=1}^{n-1} \text{full\_adder}(a_i, b_i, s_i, c_i, c_{i+1})
 \end{aligned}$$

Problem: **too slow**. Each  $c_i$  can only be computed after all of  $c_{i-1}, \dots, c_0$  have been computed

Delay:  $2n + 2$  time units for  $n$ -bit numbers

## A carry-look-ahead $n$ -adder

Compute all of  $c_{n-1}, \dots, c_0$  (and  $cout$ ) **concurrently**

**First step:** given  $a_{n-1} \dots a_0$  and  $b_{n-1} \dots b_0$ , identify the positions  $i \in [0, n - 1]$  that are

- **Generating:**  $c_{i+1} \equiv 1$  independently of  $c_i$ .  
These are the positions such that  $1 = g_i \equiv \text{and}(a_i, b_i)$ .
- **Propagating:**  $c_{i+1} \equiv c_i$ , i.e.,  $c_i$  is 'propagated' to  $c_{i+1}$ .  
These are the positions such that  $1 = p_i \equiv \text{xor}(a_i, b_i)$

Observe: all  $g_i, p_i$  can be computed simultaneously

## A carry-look-ahead $n$ -adder


**Second step:** compute the  $c_i$ 's by

$$c_i \equiv g_i \vee (p_i \wedge g_{i-1}) \vee (p_i \wedge p_{i-1} \wedge g_{i-2}) \vee \dots \vee (p_i \wedge p_{i-1} \wedge \dots \wedge g_0)$$


**Logarithmic delay in  $n$**  using balanced  $\vee$ -trees and  $\wedge$ -trees.

Delay for 64 bits: 23-56 units (instead of 130)
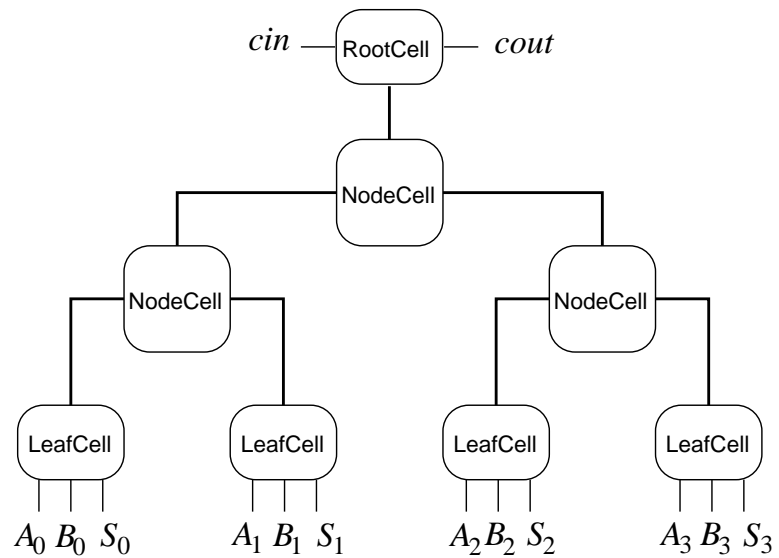
## Description of the circuit (for 4 bits)




## Description of the circuit II

 


LeafCell circuit

## Description of the circuit III

 


$\otimes$  circuit

## Description of the circuit IV

 

NodeCell circuit

 

RootCell circuit

Check validity of

$$\text{adder}_n(a_0, \dots, a_{n-1}, b_0, \dots, b_{n-1}, s_0, \dots, s_{n-1}, \text{cin}, \text{cout})$$

$\Leftrightarrow$

$$\text{cla}_n(a_0, \dots, a_{n-1}, b_0, \dots, b_{n-1}, s_0, \dots, s_{n-1}, \text{cin}, \text{cout})$$

Results of the [SAT 2002 competition](#) on a variant of this problem:

- Task was to compare 2, 4, 8, ..., 256 bits adders (8 problems)
- From 26 variables and 70 3CNF clauses to 4584 variables and 13226 clauses
- Fastest solver (Zchaff) checked all 8 problems in 14 seconds
- More info at [www.satcompetition.org](http://www.satcompetition.org)

Rule-of-thumb: circuits with some hundreds of gates are routinely solved