

Quantified Boolean Logic

Extension of propositional logic with **boolean quantifiers**.

We write

$\exists A F$ as an abbreviation of $F[A/0] \vee F[A/1]$

$\forall A F$ as an abbreviation of $F[A/0] \wedge F[A/1]$

Abbreviations can be nested, and then they are “unfolded” inside-out:

$\exists A \forall B (A \wedge B)$

abbreviates $\exists A (A \vee 0) \wedge (A \vee 1)$

which abbreviates $((0 \vee 0) \wedge (0 \vee 1)) \vee ((1 \vee 0) \wedge (1 \vee 1))$


Intuitively, $\exists A \forall B (A \wedge B)$ “means”

there exists a truth value for A such that for every truth value for B the formula $(A \wedge B)$ becomes true.

Modelling circuits with QBL

Gates as boolean formulas

 Stable states as satisfying truth assignments



$$\mathbf{not}(a, b) \equiv \neg a \leftrightarrow b$$


$$\mathbf{and}(a, b, c) \equiv (a \wedge b) \leftrightarrow c$$

$$\mathbf{or}(a, b, c) \equiv (a \vee b) \leftrightarrow c$$

$$\mathbf{xor}(a, b, c) \equiv ((\neg a \wedge b) \vee (a \wedge \neg b)) \leftrightarrow c$$

Combining gates means combining formulas

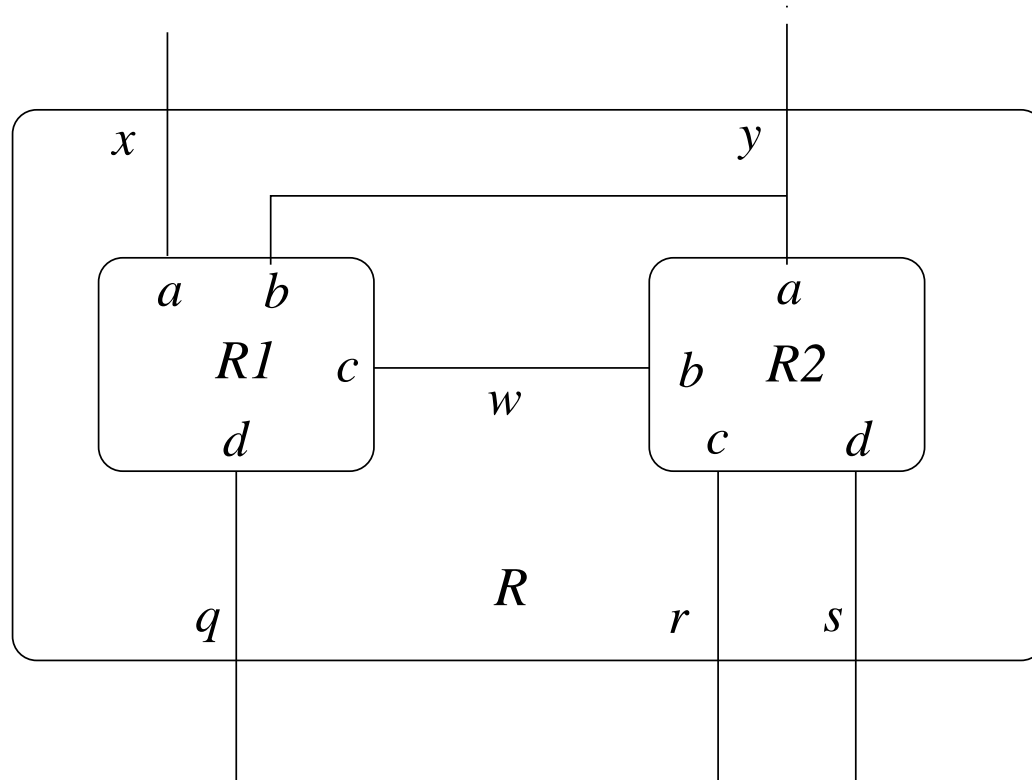
Combine gates with \wedge , \exists (and renaming of atomic formulas)



$$R(x, y, q, r, s) = \exists w R_1(x, y, w, q) \wedge R_2(y, w, r, s)$$

A full adder
 
$$\begin{array}{r} \text{cout} \quad \text{cin} \quad \dots \\ \dots \quad a \quad \dots \\ + \quad \dots \quad b \quad \dots \\ \hline \dots \quad s \quad \dots \end{array}$$




$\text{full_adder}(a, b, s, \text{cin}, \text{cout}) \equiv$

$$\exists w_1 \exists w_2 \exists w_3 \mathbf{xor}(a, b, w_1) \wedge \mathbf{xor}(w_1, \text{cin}, s) \wedge \mathbf{and}(a, b, w_2) \wedge \\ \mathbf{and}(\text{cin}, w_1, w_3) \wedge \mathbf{or}(w_3, w_2, \text{cout})$$

A n -bit ripple-carry adder

$$\begin{array}{r} c_2 \quad c_1 \quad cin \quad (= 0) \\ a_2 \quad a_1 \quad a_0 \\ + \quad b_2 \quad b_1 \quad b_0 \\ \hline cout \quad s_2 \quad s_1 \quad s_0 \end{array}$$

 Wire together n 1-bit adders where i -th carry-out is $i+1$ -st carry-in, first carry is the carry-in and last is the carry-out.



We obtain the formula

$$\begin{aligned} \mathbf{adder}_n(a_0, \dots, a_{n-1}, b_0, \dots, b_{n-1}, s_0, \dots, s_{n-1}, \mathit{cin}, \mathit{cout}) \equiv \\ \exists c_0 \exists c_1 \dots \exists c_n (c_0 \leftrightarrow \mathit{cin}) \wedge (c_n \leftrightarrow \mathit{cout}) \wedge \\ \bigwedge_{i=1}^{n-1} \mathbf{full_adder}(a_i, b_i, s_i, c_i, c_{i+1}) \end{aligned}$$

Problem: **too slow**. Each c_i can only be computed after all of c_{i-1}, \dots, c_0 have been computed

Delay: $2n + 2$ time units for n -bit numbers

A carry-look-ahead n -adder

Compute all of c_{n-1}, \dots, c_0 (and c_{out}) **concurrently**

First step: given $a_{n-1} \dots a_0$ and $b_{n-1} \dots b_0$, identify the positions $i \in [0, n - 1]$ that are

- **Generating:** $c_{i+1} \equiv 1$ independently of c_i .
These are the positions such that $1 = g_i \equiv \mathbf{and}(a_i, b_i)$.
- **Propagating:** $c_{i+1} \equiv c_i$, i.e., c_i is 'propagated' to c_{i+1} .
These are the positions such that $1 = p_i \equiv \mathbf{xor}(a_i, b_i)$

Observe: all g_i, p_i can be computed simultaneously

A carry-look-ahead n -adder


Second step: compute the c_i 's by

$$c_i \equiv g_i \vee (p_i \wedge g_{i-1}) \vee (p_i \wedge p_{i-1} \wedge g_{i-2}) \vee \dots \vee (p_i \wedge p_{i-1} \wedge \dots \wedge g_0)$$


Logarithmic delay in n using balanced \vee -trees and \wedge -trees.

Delay for 64 bits: 23-56 units (instead of 130)

Description of the circuit (for 4 bits)

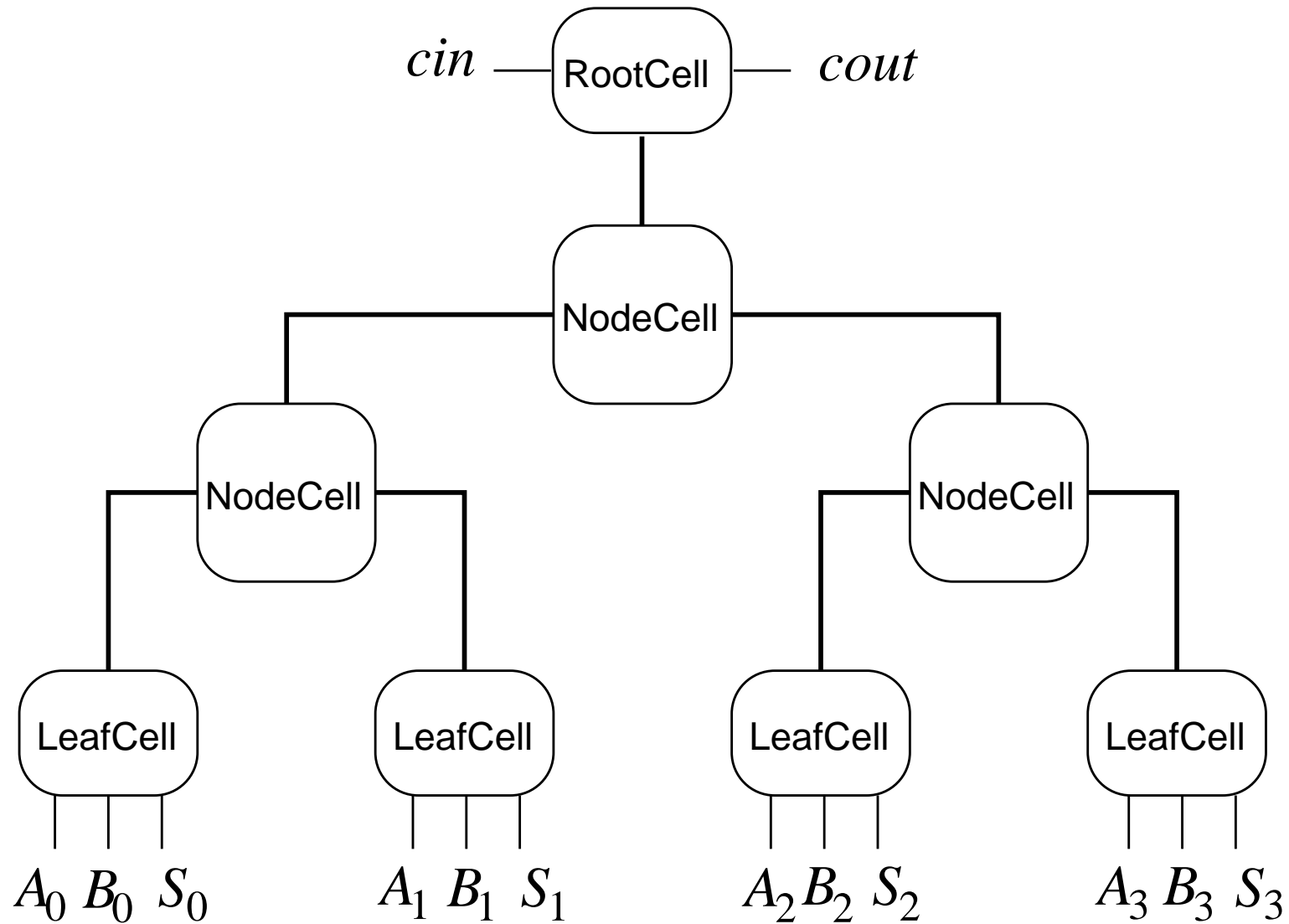


Description of the circuit II

 


LeafCell circuit

Description of the circuit III

 


⊗ circuit

Description of the circuit IV

 

NodeCell circuit

Description of the circuit V

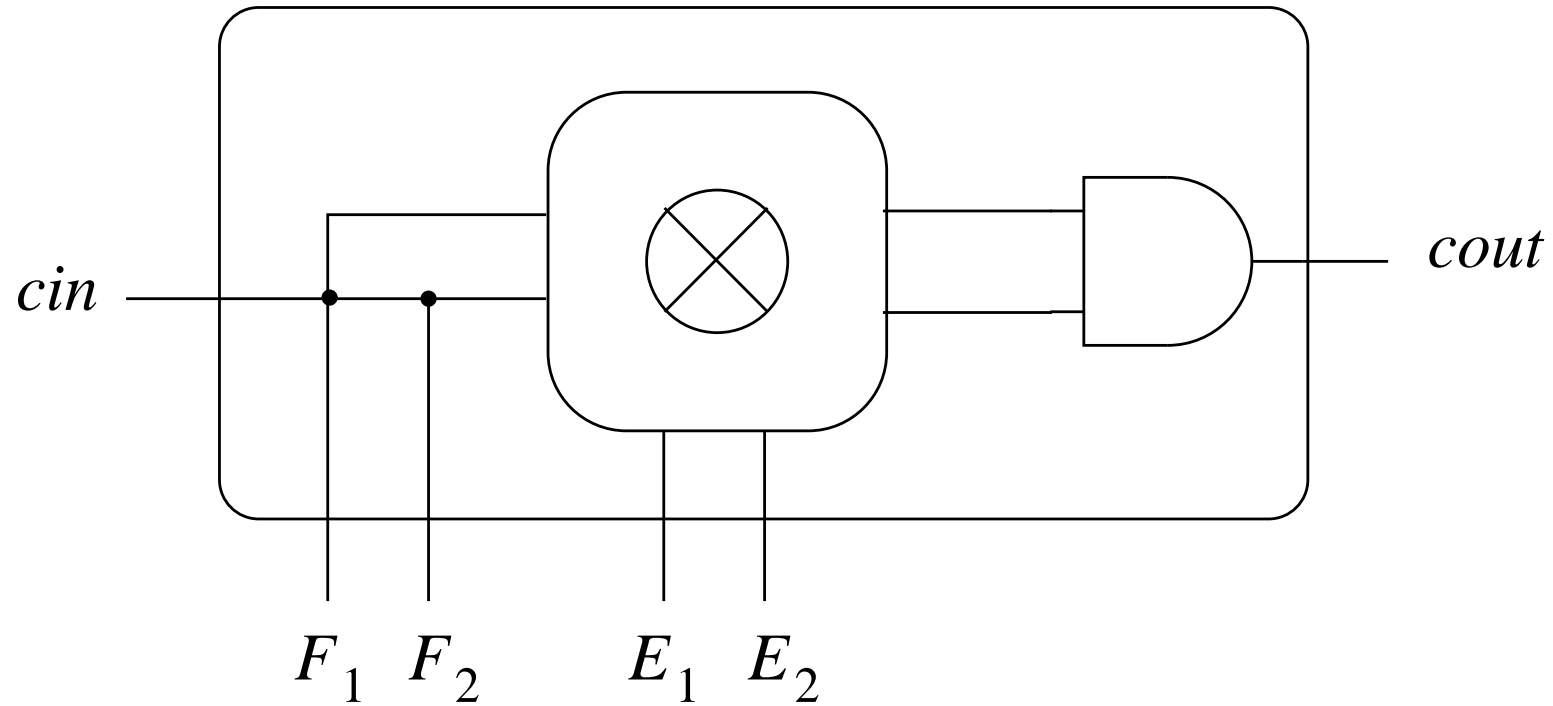

RootCell circuit

Verification of the carry-look-ahead n -adder

Check validity of

$$\text{adder}_n(a_0, \dots, a_{n-1}, b_0, \dots, b_{n-1}, s_0, \dots, s_{n-1}, \text{cin}, \text{cout})$$
$$\Leftrightarrow$$
$$\text{cla}_n(a_0, \dots, a_{n-1}, b_0, \dots, b_{n-1}, s_0, \dots, s_{n-1}, \text{cin}, \text{cout})$$

Results of the [SAT 2002 competition](#) on a variant of this problem:

- Task was to compare 2, 4, 8, ..., 256 bits adders (8 problems)
- From 26 variables and 70 3CNF clauses to 4584 variables and 13226 clauses
- Fastest solver (Zchaff) checked all 8 problems in 14 seconds
- More info at www.satcompetition.org

Rule-of-thumb: circuits with some hundreds of gates are routinely solved